

CSE250  
ASSIGNMENT 1 (SUMMER 2023)  
SECTION 05, 06, 22

**Instructions**


- There are **14 Questions** covering different topics in this assignment.
- Try to solve them and understand them properly.
- **Make a PDF file** containing all your answers and submit it **before 11:59 PM, 20<sup>th</sup> July, 2023**.
- Your Cover page must be **Handwritten** and should contain your **Name, ID, Course Code, Section, whom you are submitting to, and submission date**.
- The file naming convention is as follows:  
**NAME\_ID\_ASSIGNMENT\_1\_CSE250.pdf**.
- Also, **keep the hard copy**. We may need to submit that to the authority depending on the instructions.

Remember, if you can't solve or even attempt all the questions, **No Problem!** But you must try. Try to solve at least some questions from each topic. If you can't solve a question by yourself, discuss specific details in the **Queries** channel in Discord. Your classmates may help you and vice-versa. But don't give your answers to anybody directly. **Any kind of plagiarism will result in a harsh penalty. Good luck with your Exams!**


## Questions

### Series-Parallel

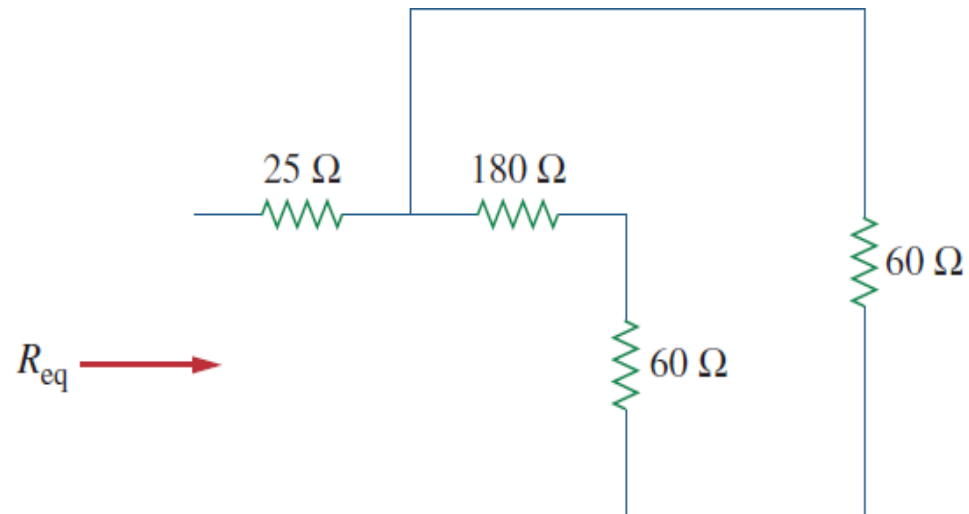
1. Find  $R_{eq}$  for the circuit given below:



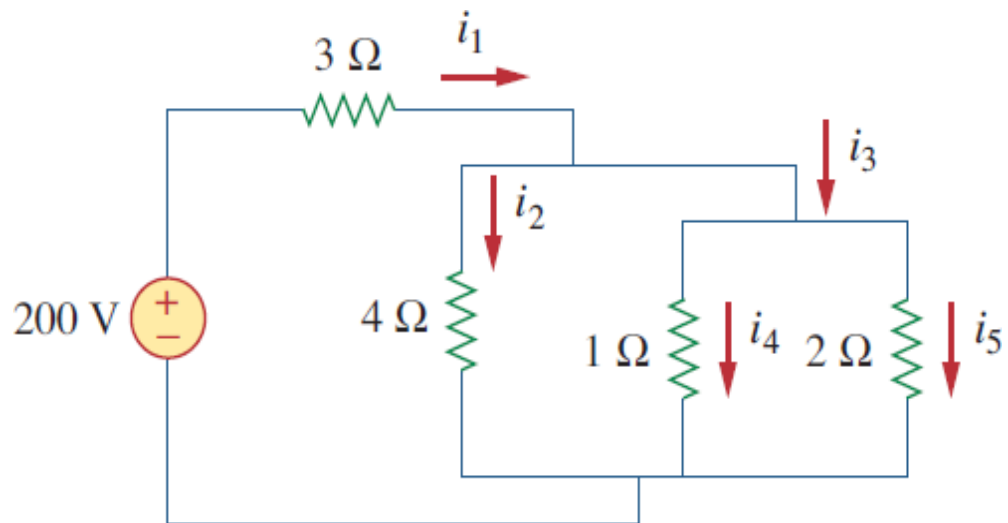2. For the circuit below, determine  $i_1$  to  $i_5$ .




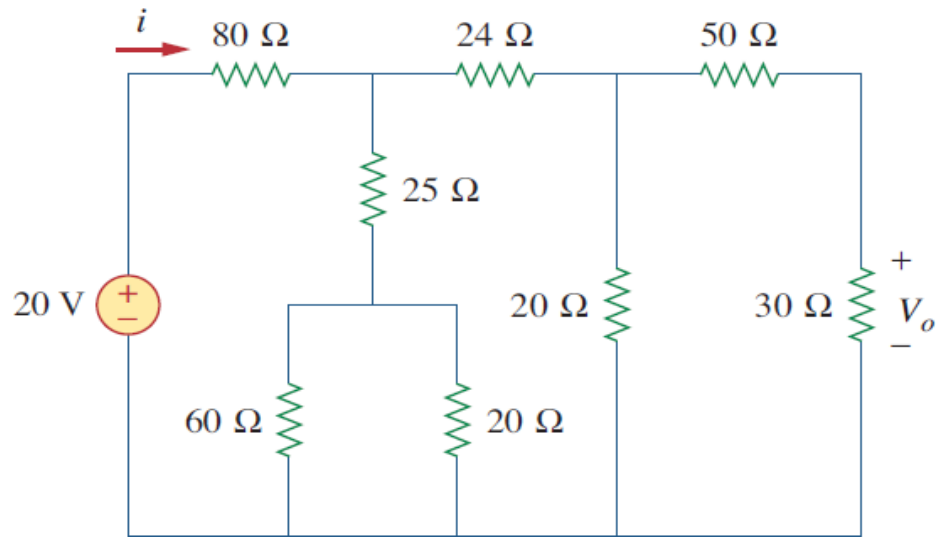3. Find  $i$  and  $V_o$  in the circuit below:




### Nodal Analysis

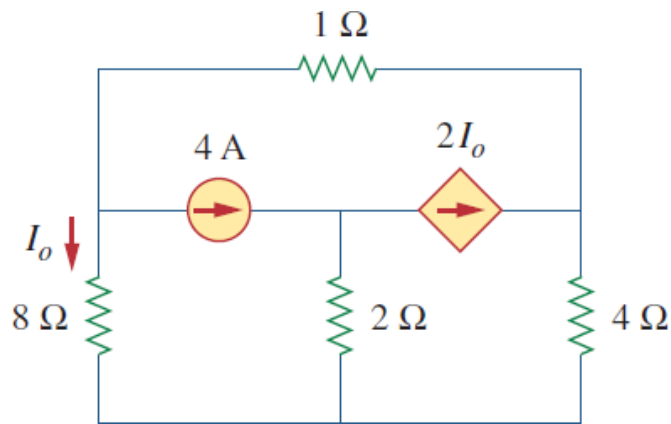
4. Find  $I_o$  in the circuit shown below:



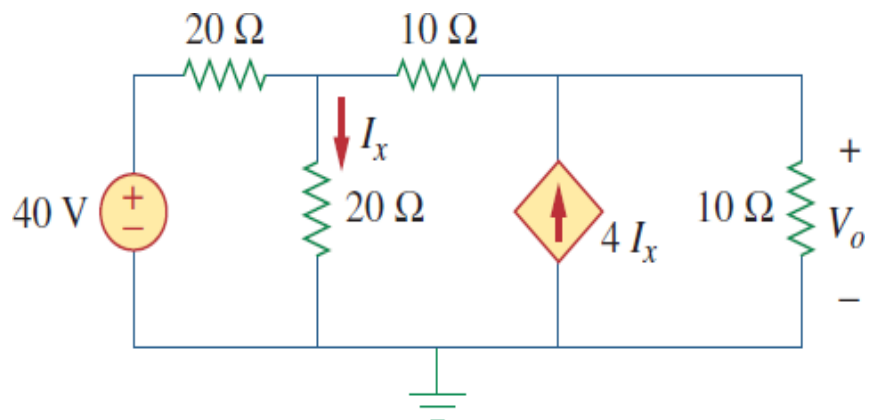
5. Using nodal analysis, determine  $V_o$  in the circuit below:



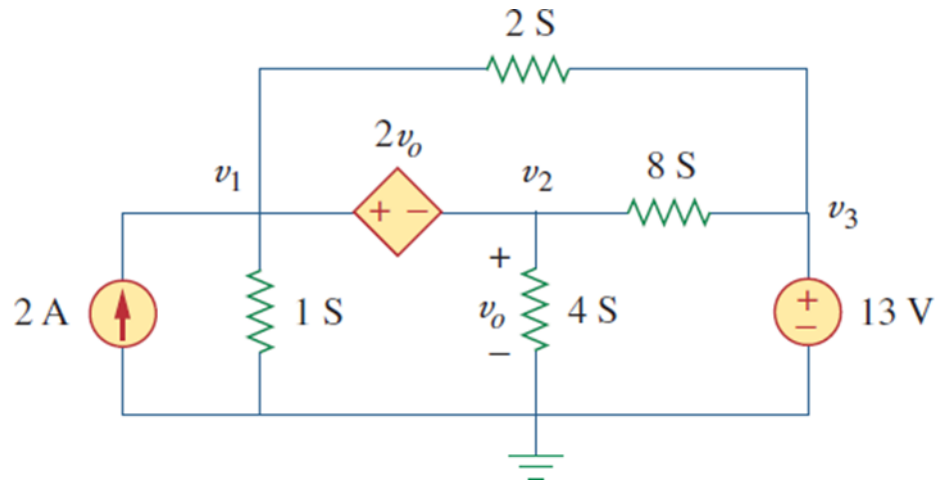
6. Determine voltages  $v_1$  through  $v_3$  in the circuit shown below using nodal analysis. [Use  $\Omega$  instead of S]



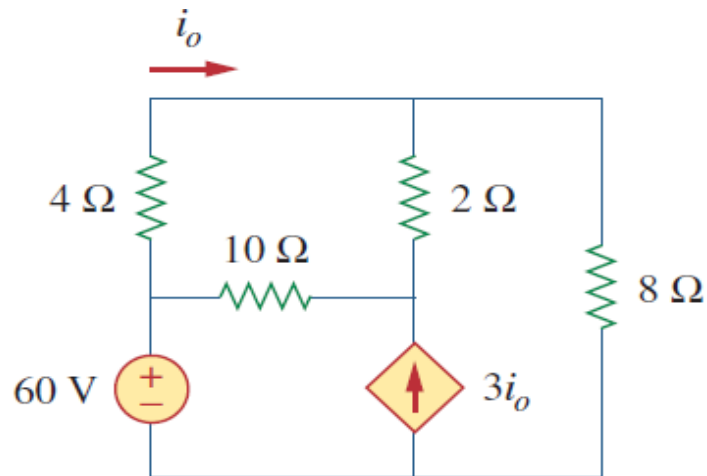
7. Using nodal analysis, find current  $i_o$  in the circuit given below:



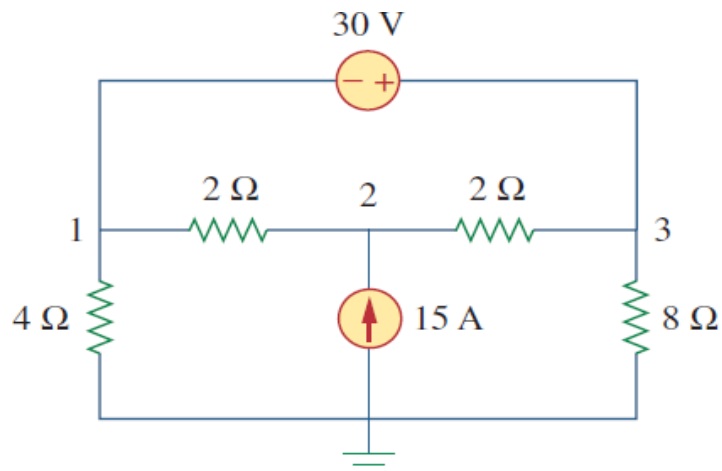8. Determine the node voltages in the circuit shown below using nodal analysis.




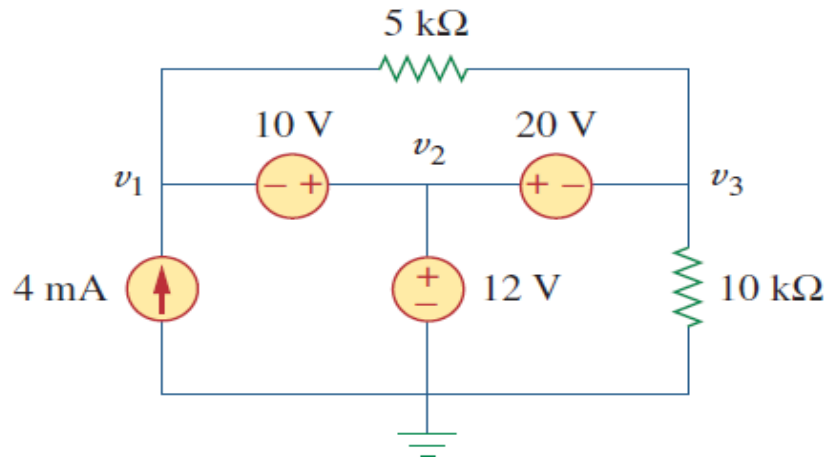9. Obtain the node voltages from the circuit shown below:




### Superposition Principle

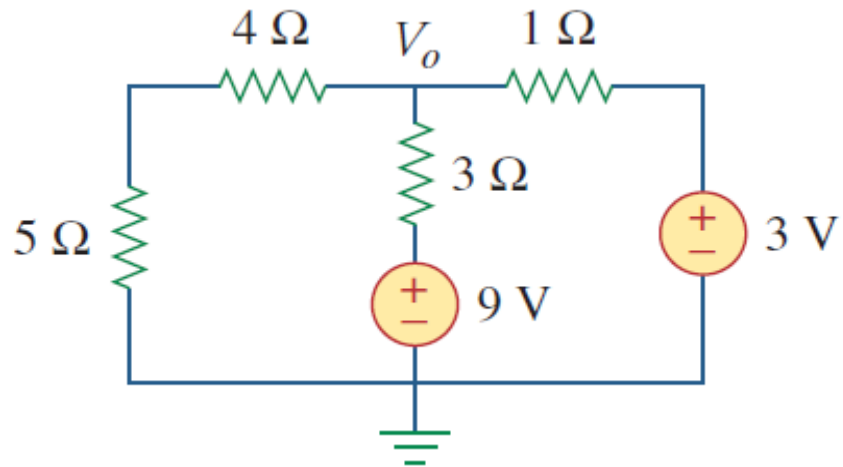
10. Find  $V_o$  using the Superposition Principle.



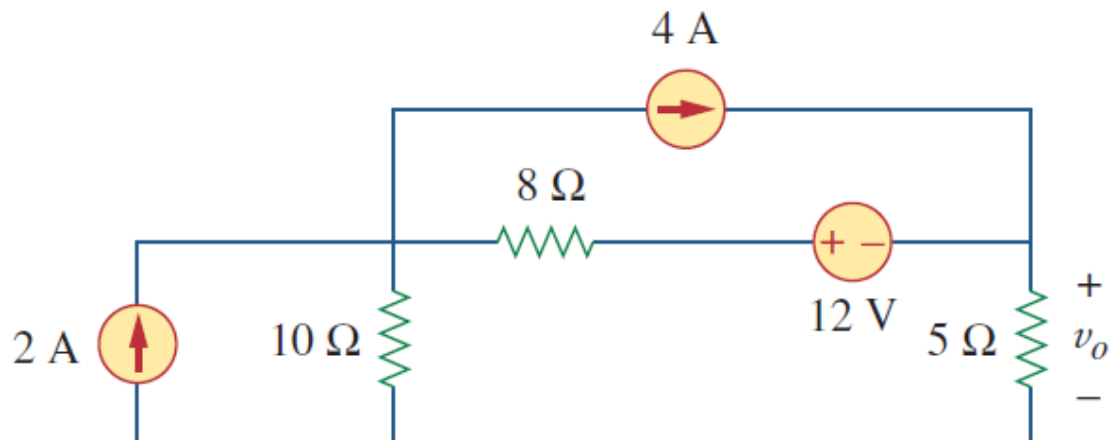
11. Find  $V_o$  using Superposition Principle.



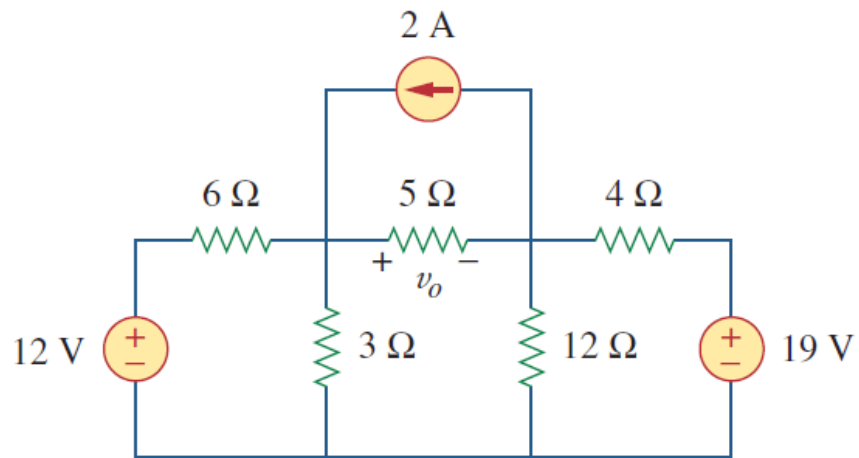12. Find  $\mathbf{v_o}$  using Superposition Principle.



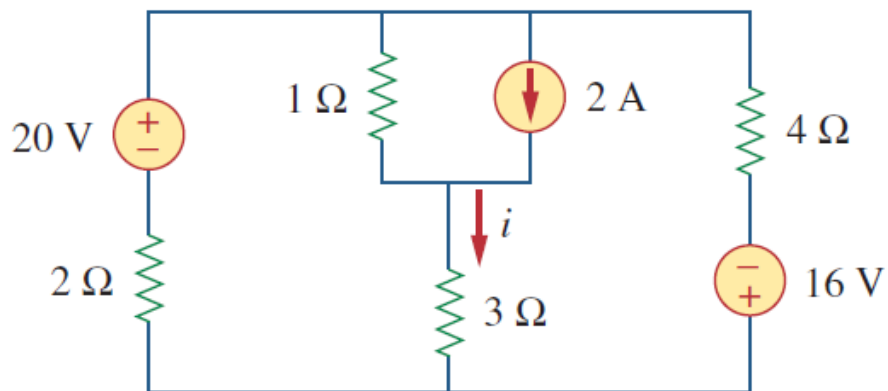13. Find  $\mathbf{i}$  using the Superposition Principle.



14. Find  $\mathbf{v_o}$  and  $\mathbf{i_o}$  using the Superposition Principle.

