
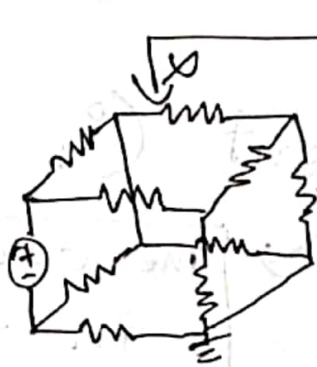


Week 4 Part 2 Mesh Analysis

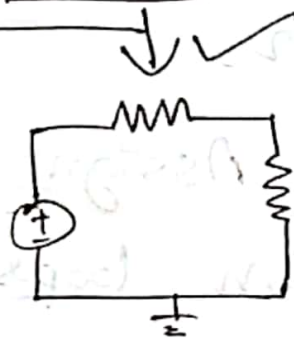
- Works using ~~KCL~~ \rightarrow KVL ✓
- Component Equation for Resistance $\Rightarrow \boxed{\Delta V = IR}$
- Applicable in case of Planar circuits.



Non-Planar



Planar

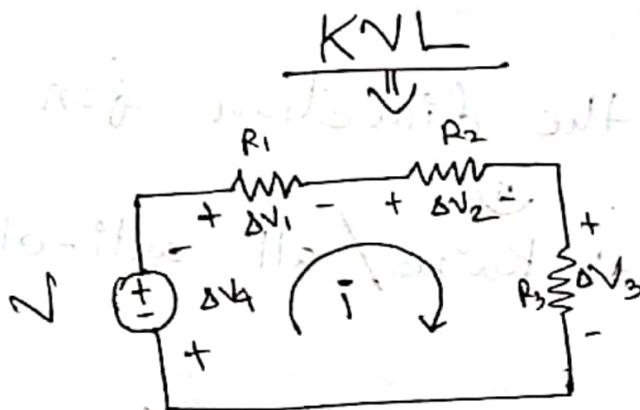

$$\Rightarrow \sum \Delta V = 0$$

$$\Rightarrow \Delta V_1 + \Delta V_2 + \Delta V_3 + \Delta V_4 = 0$$

$$\Rightarrow iR_1 + iR_2 + iR_3 - V = 0$$

□ Current (i) direction
is clockwise or anti-clockwise
in all loops

Steps → Of Mesh Analysis

Step-1

Find out the number of loops in the circuit → n

Circuit → Assign a number (~~0 to $n-1$~~)
↳ (1 to n).

Step-2

Assign a current (i_1 to i_n) to each loop.

The current circulating in that loop.

Step-3


Select the direction for each current.

Take all clockwise / all anti-clockwise.

Step-4

Write component equations for all the

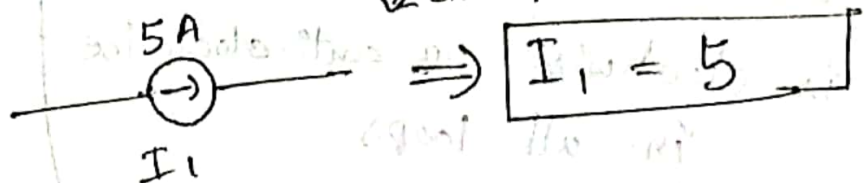
Current Sources → [Current = Labeled value]




Step-5

Determine the voltage drop across each resistor for each loops using Ohm's Law.

$$\Delta V = IR$$

•  $\Rightarrow \Delta V = i_1 \cdot 2$

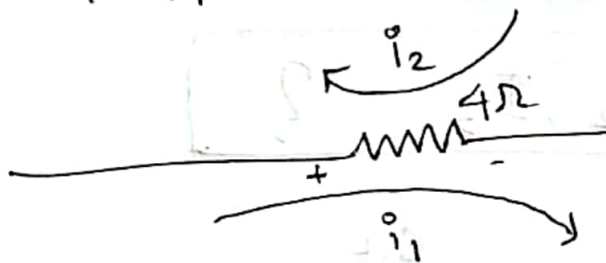•  $\Rightarrow \Delta V = (i_1 - i_2) \cdot 4$

Step-6

Write KVL equations for all the loops/meshes and supermeshes with unknown current.


\Downarrow
[Not needed in loops with known value of i]

Step-7

Solve all the equations to find all the mesh currents. [Calculation / By substitution]


Mesh Analysis

1

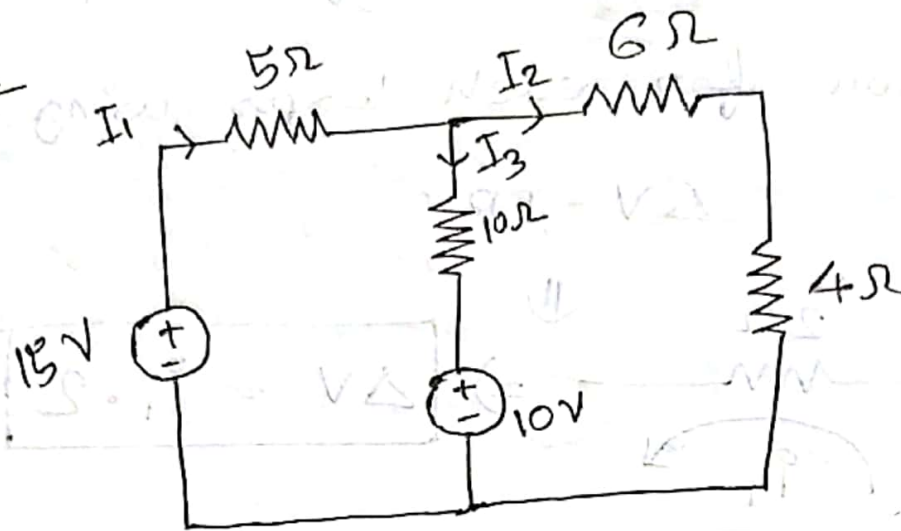


$$I_1, I_2, I_3 = ?$$

Step-1

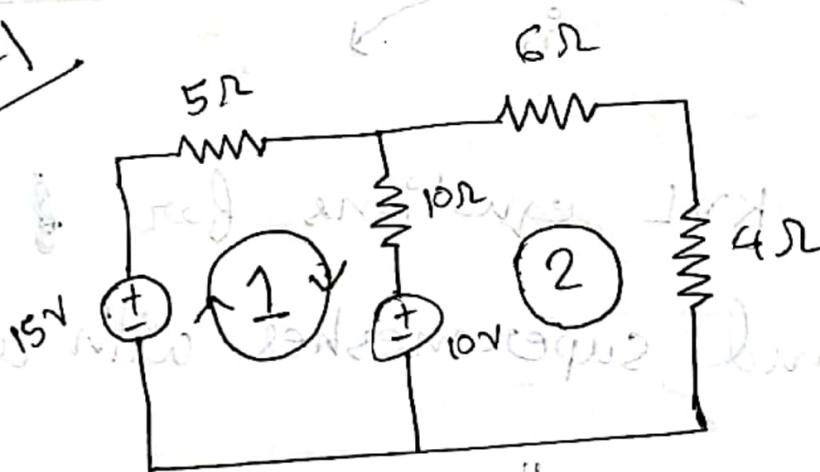

Step-2
+3

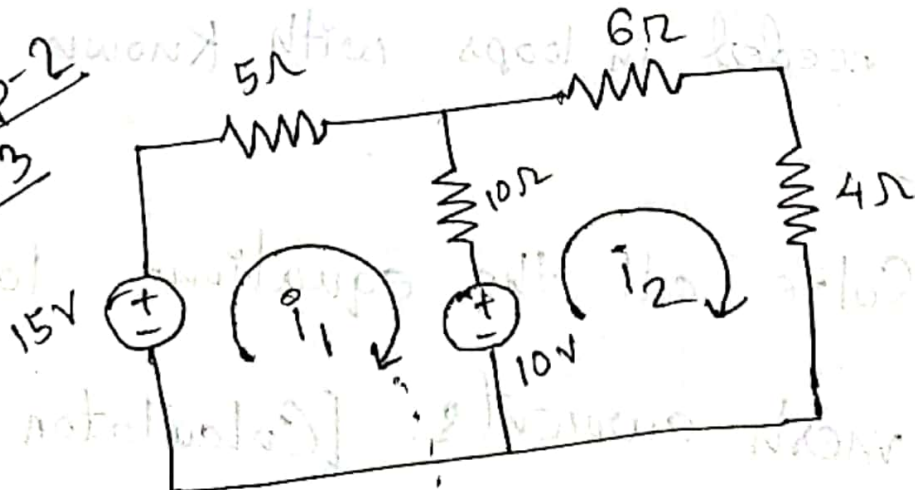


→ Clockwise

Step-4

No current sources

Step-5


Loop-1

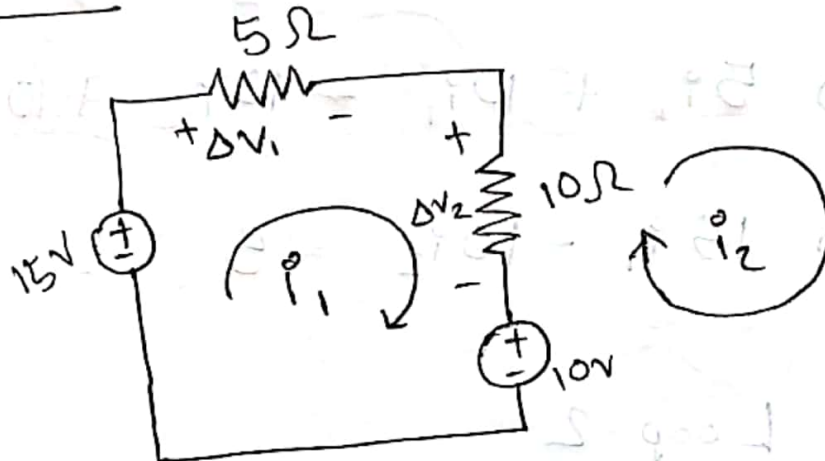

$$\Delta V_1 = i_1 \times 5 = 5i_1$$

$$\Delta V_2 = (i_1 - i_2) \times 10 = 10i_1 - 10i_2$$

Loop-2

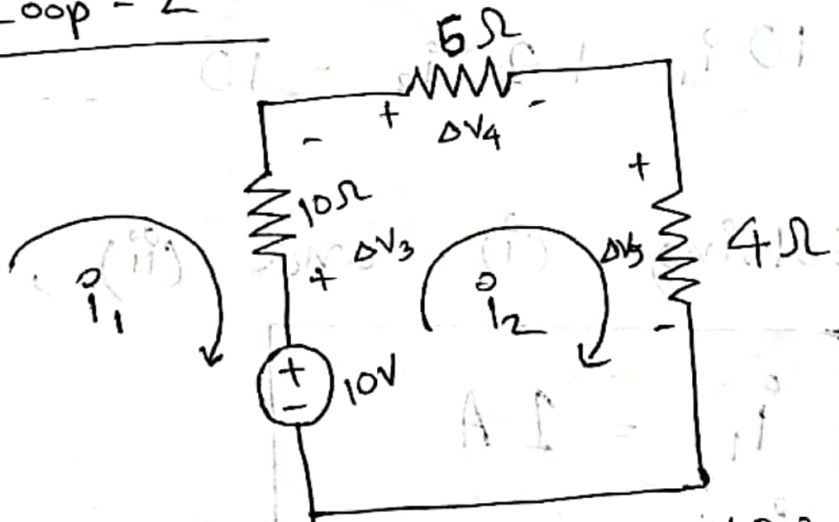

$$\Delta V_3 = (i_2 - i_1) \times 10 = 10i_2 - 10i_1$$

$$\Delta V_4 = i_2 \times 5 = 5i_2$$

$$\Delta V_5 = i_2 \times 4 = 4i_2$$

Step-6

Loop-1

$$\Delta V_1 + \Delta V_2 + 10 - 15 = 0$$

$$\Rightarrow 5i_1 + 10i_1 - 10i_2 + 10 - 15 = 0$$

$$\Rightarrow 15i_1 - 10i_2 = 5 \quad \text{--- (i)}$$

Loop-2

$$\Delta V_3 + \Delta V_4 + \Delta V_5 + 10 = 0$$

$$\Rightarrow 10i_2 - 10i_1 + 6i_2 + 4i_2 - 10 = 0$$

$$\Rightarrow -10i_1 + 20i_2 = 10 \quad \text{--- (ii)}$$

Step-7

Solving (i) and (ii),

i_1	$= 1 \text{ A}$
i_2	$= 1 \text{ A}$

$I_1, I_2, I_3?$

$$I_1 = i_1$$

| From circuit diagram |

$$\therefore I_1 = 1 \text{ A}$$


$$I_2 = i_2$$

$$\therefore I_2 = 1 \text{ A}$$

$$I_3 = i_1 - i_2$$

$$\therefore I_3 = (1 - 1) \text{ A}$$


$$\therefore I_3 = 0 \text{ A}$$

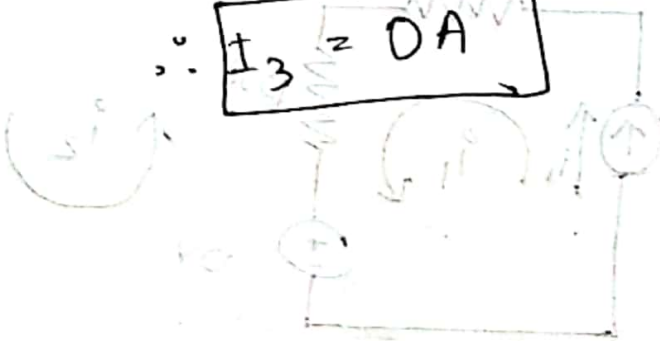

(Am.)

$$I = 1 \text{ A}$$

Mesh Analysis with Current Source

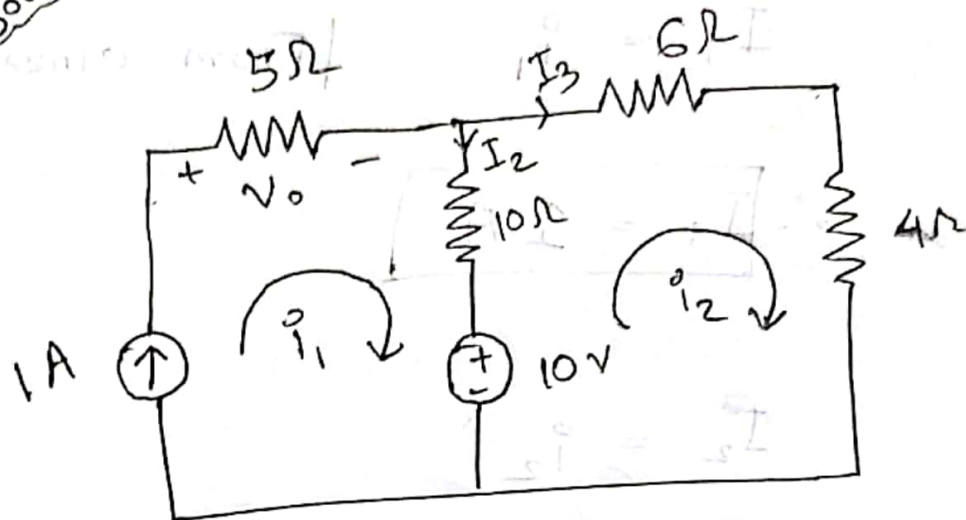


Step 1-3

Step-4

There is a current source in

Loop - 1,

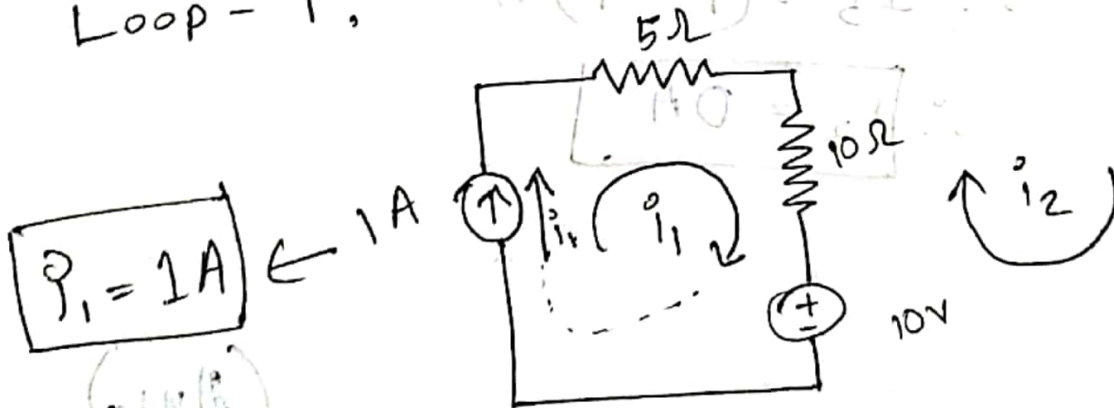

Step-6

Loop - 1

$$i_1 = 1$$

--- (i)

Loop-2

Like before,

$$-10i_1 + 20i_2 = 10 \quad \dots \dots (ii)$$

Step-7

$$\Rightarrow -10 \cdot 1 + 20i_2 = 10$$

$$\Rightarrow 20i_2 = 10 + 10 = 20$$

$$\Rightarrow i_2 = \frac{20}{20}$$

$$\therefore i_2 = 1$$

$$\therefore i_1 = 1 \text{ A}, \quad i_2 = 1 \text{ A.}$$

V_o

$$V_o = i_1 \cdot 5 \text{ V}$$

| From circuit |

$$= 1 \cdot 5 \text{ V}$$

$$= \boxed{5 \text{ V}}$$

I_2

$$I_2 = i_1 - i_2 \quad | \text{ From circuit} |$$

$$= \boxed{0 \text{ A}}$$

I_3


$$I_3 = i_2 = \boxed{1 \text{ A}}$$

(Ans.)

Supermesh

↳ A Current Source in between two loops → Those two loops (Meshes) together become Supermesh.

Practise Example

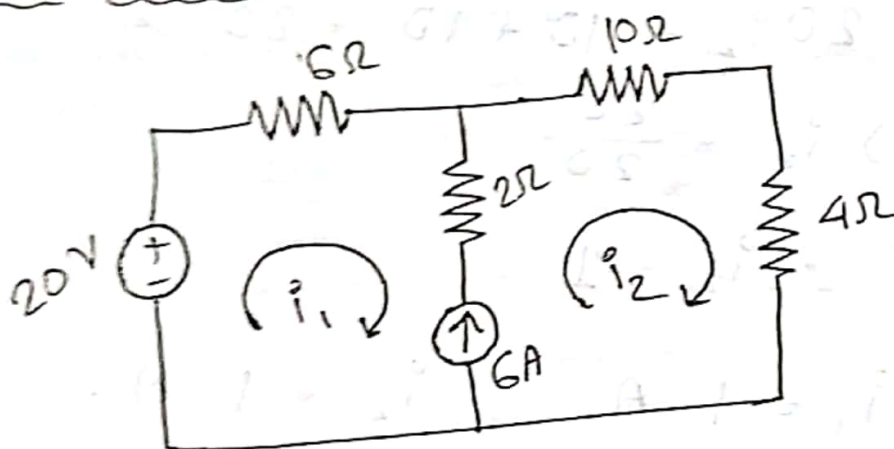

Step-4

6A Current source in between loop 1 and loop 2 → Supermesh.

$$i_2 - i_1 = 6 \quad \text{--- (i)}$$

Step-5


$$\Delta V_{6\Omega} = 6i_1$$

$$\Delta V_{10\Omega} = 10i_2$$

$$\Delta V_{4\Omega} = 4i_2$$

Step-6

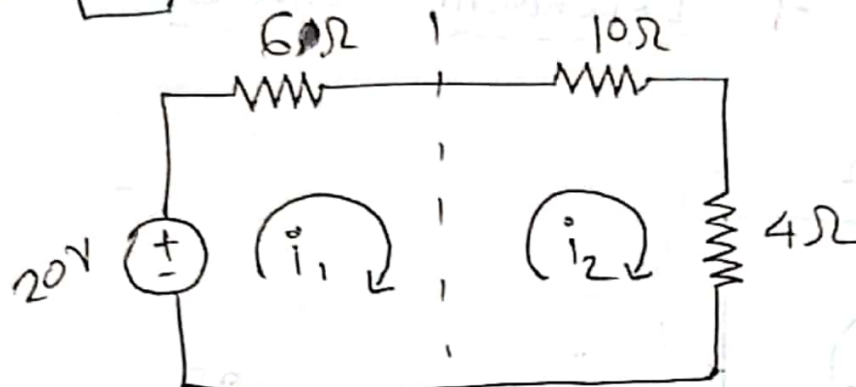Ignore all common components betⁿ those two loops.



Mesh Eqn.

$$-20 + 6i_1 + 10i_2 + 4i_2 = 0$$


$$\Rightarrow 6i_1 + 14i_2 = 20 \quad \text{--- (ii)}$$

Step-7

Solving (i) & (ii),

$$i_1 = -3.2 \text{ A} \quad , \quad i_2 = 2.8 \text{ A}$$

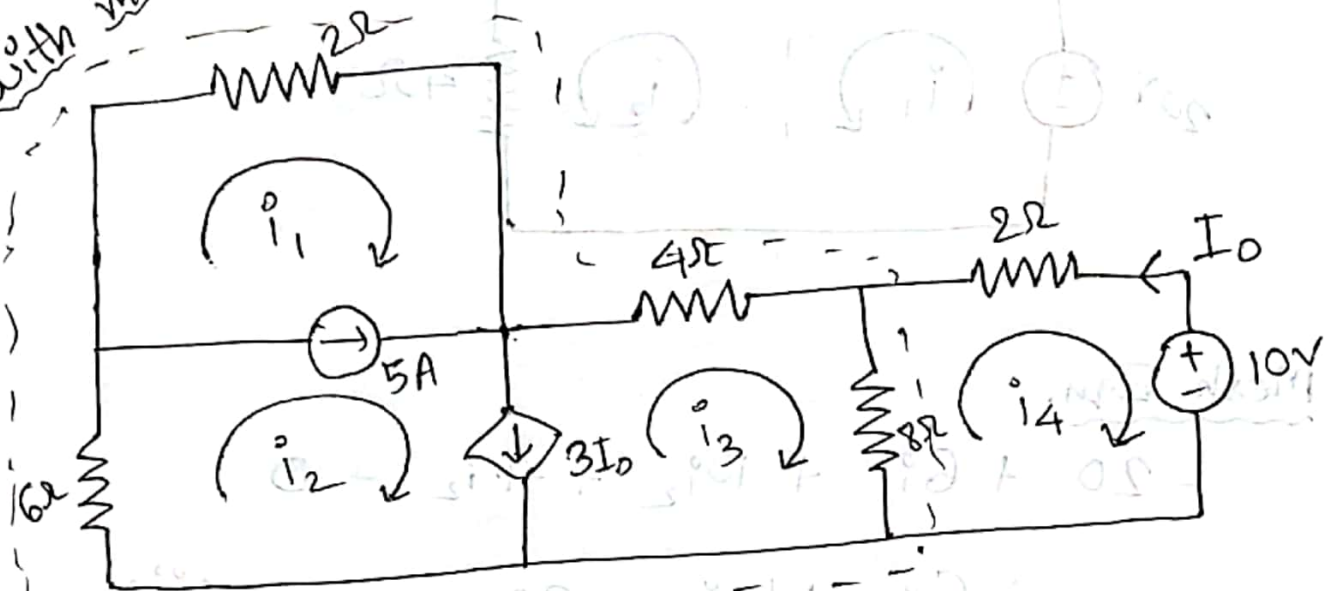Supermesh
with more than two loops + Dependent Source



→ Bigger Supermesh
created by two Supermeshes

Step-4

$$i_2 - i_1 = 5 \text{ A} \quad \text{--- (i)}$$

$$i_2 - i_3 = 3I_0 \quad \text{--- (ii)}$$

Now, $i_4 = -I_0 \Rightarrow I_0 = -i_4$ | From Loop 4 |

$$\therefore i_2 - i_3 = -3i_4$$


$$\Rightarrow i_2 - i_3 + 3i_4 = 0 \quad \text{--- (iii)}$$

Step-5

You can skip this part now with practise ;)

Step-6

Supermesh

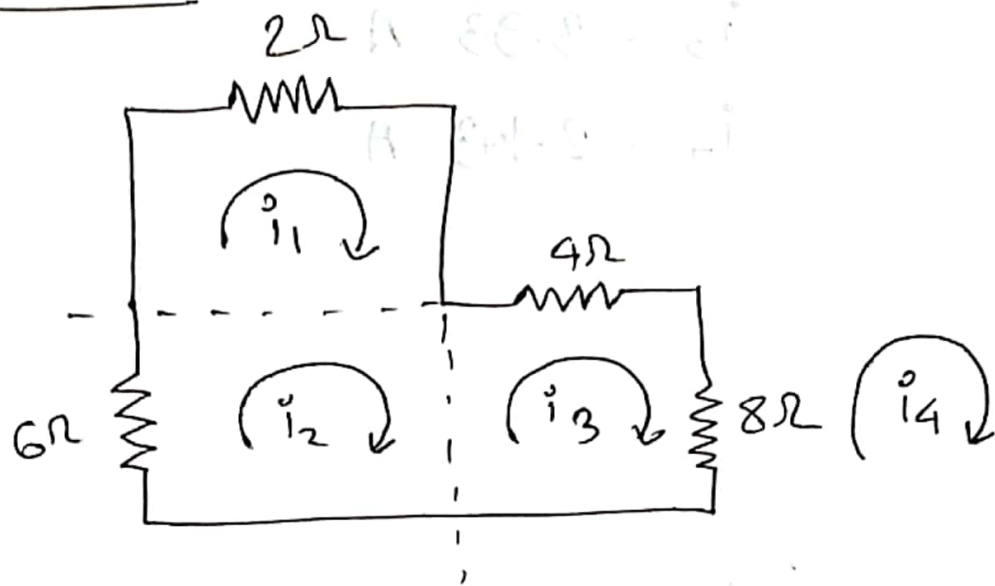

Eqn.

$$2i_1 + 6i_2 + 4i_3 + 8(i_3 - i_4) = 0$$

$$\Rightarrow 2i_1 + 6i_2 + 12i_3 - 8i_4 = 0 \quad \dots \quad (iv)$$

Loop-4

$$8(i_4 - i_3) + 2i_4 + 10 = 0$$

$$\Rightarrow 10i_4 - 8i_3 = -10 \quad \dots \quad (v)$$

Step-7


Solving i_1, i_2, i_3, i_4, v

$$i_1 = -7.5 \text{ A}$$


$$i_2 = -2.5 \text{ A}$$

$$i_3 = 3.93 \text{ A}$$


$$i_4 = 2.143 \text{ A}$$

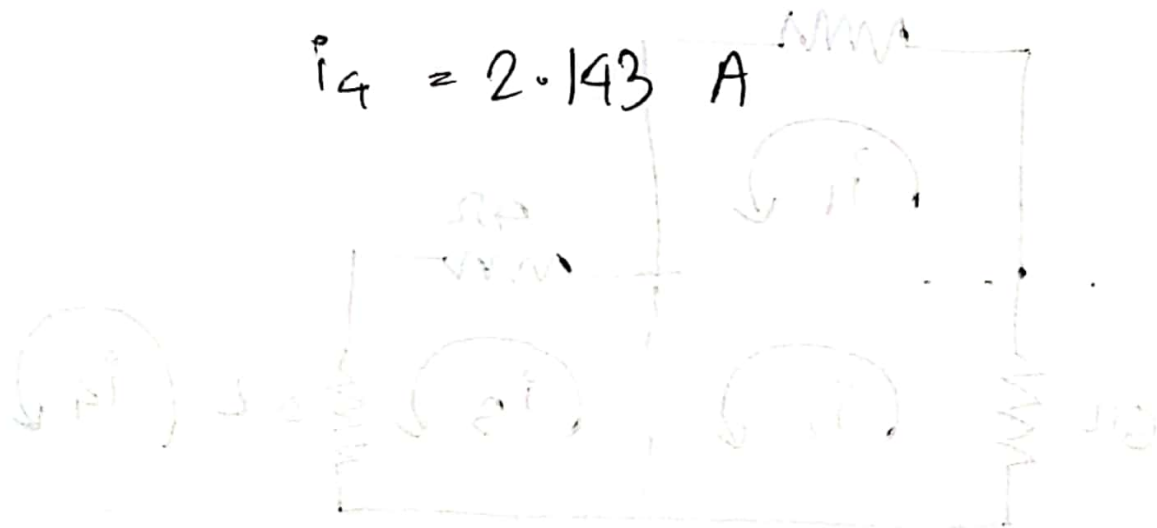


Dependent Sources

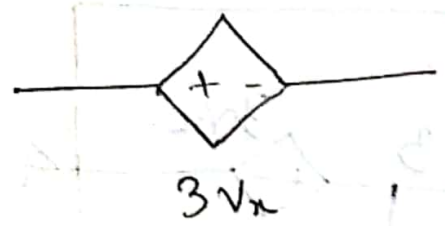•  $3V_x$ \rightarrow Voltage Controlled Voltage Source

•  $3I_x$ \rightarrow Current Controlled Voltage Source

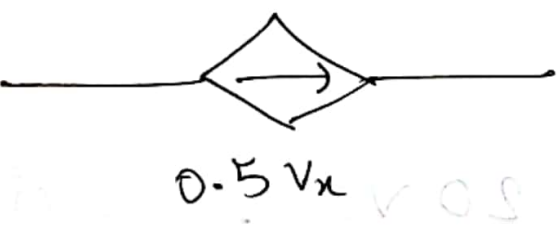•  $0.5V_x$ \rightarrow Voltage Controlled Current Source

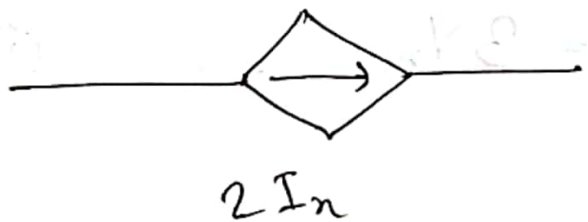•  $2I_x$ \rightarrow Current Controlled Current Source


How to Deal with them?

Simply replace V_x/I_x with the corresponding component equation from the circuit.

Example: Previous One.

They also form Supernodes and Supernodes.

Example for Nodal Analysis

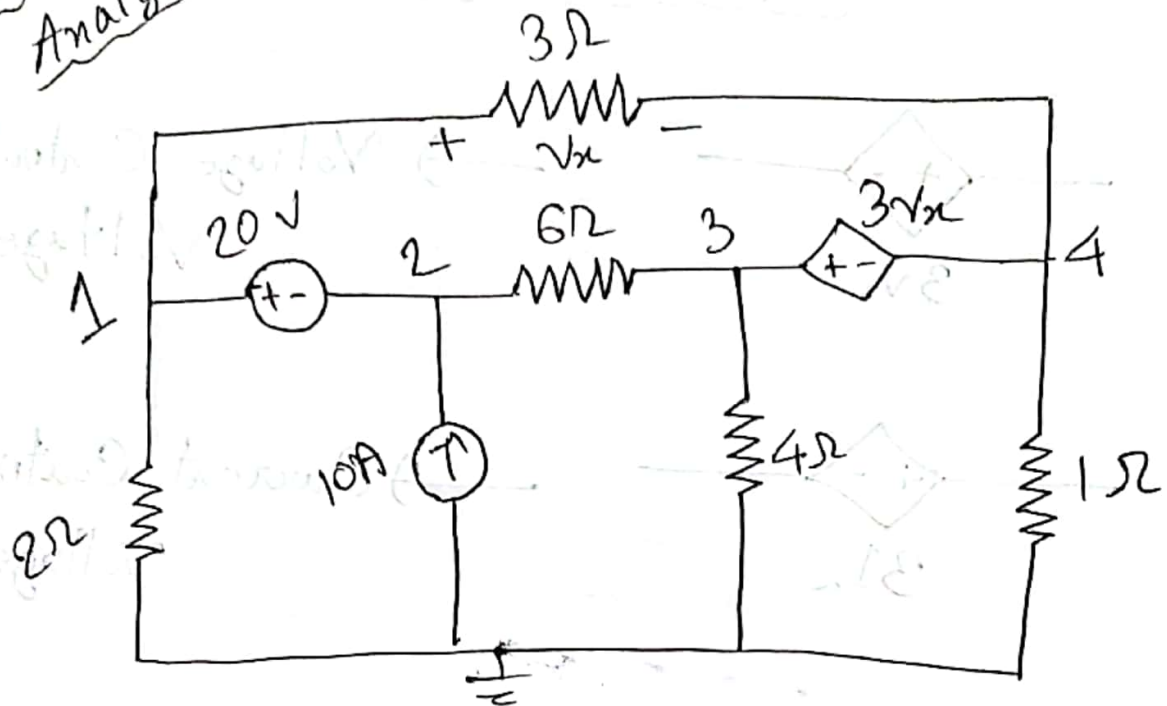

Step-2

$$V_1 - V_2 = 20 \text{ V} \quad \text{--- (i)}$$

$$V_3 - V_4 = 3V_x \quad \text{--- (ii)}$$

Now, $V_x = V_1 - V_4$

$$V_3 - V_4 = 3(V_1 - V_4)$$

$$\Rightarrow 3V_1 - V_3 + 2V_4 = 0 \quad \text{--- (iii)}$$

Step-3

No need anymore I guess?

Step-4

SuperNode 1-2

$$V_1 \left(\frac{1}{2} + \frac{1}{3} \right) - \frac{V_4}{3} + V_2 \left(\frac{1}{6} \right) - 10 = 0$$

----- (iv)

SuperNode 3-4

$$V_3 \left(\frac{1}{6} + \frac{1}{4} \right) - \frac{V_2}{6} + V_4 \left(1 + \frac{1}{3} \right) - \frac{V_1}{3} = 0$$

----- (v)

Step-5

Solve (i), (iii), (iv), (v) . to get

$V_1, V_2, V_3, V_4.$