

CSE250  
ASSIGNMENT 2 (SUMMER 2023)  
SECTION 05, 06, 22

**Instructions**


- There are **10 Questions** covering different topics in this assignment.
- Try to solve them and understand them properly.
- **Make a PDF file** containing all your answers and submit it **before 11:59 PM, 20<sup>th</sup> July, 2023**.
- Your Cover page must be **Handwritten** and should contain your **Name, ID, Course Code, Section, whom you are submitting to, and submission date**.
- The file naming convention is as follows:  
**NAME\_ID\_ASSIGNMENT\_2\_CSE250.pdf**.
- Also, **keep the hard copy**. We may need to submit that to the authority depending on the instructions.

Remember, if you can't solve or even attempt all the questions, **No Problem!** But you must try. Try to solve at least some questions from each topic. If you can't solve a question by yourself, discuss specific details in the **Queries** channel in Discord. Your classmates may help you and vice-versa. But don't give your answers to anybody directly. **Any kind of plagiarism will result in a harsh penalty. Good luck with your Exams!**


## Questions

### Mesh Analysis

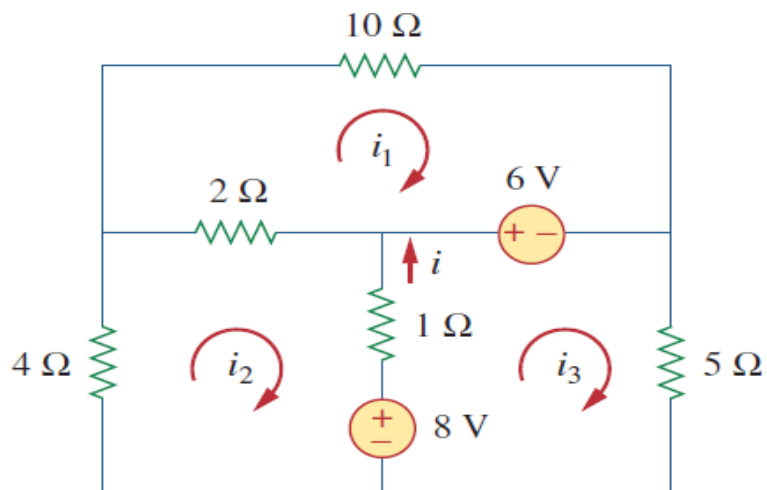
1. Apply mesh analysis to find  $i$  in the circuit below.



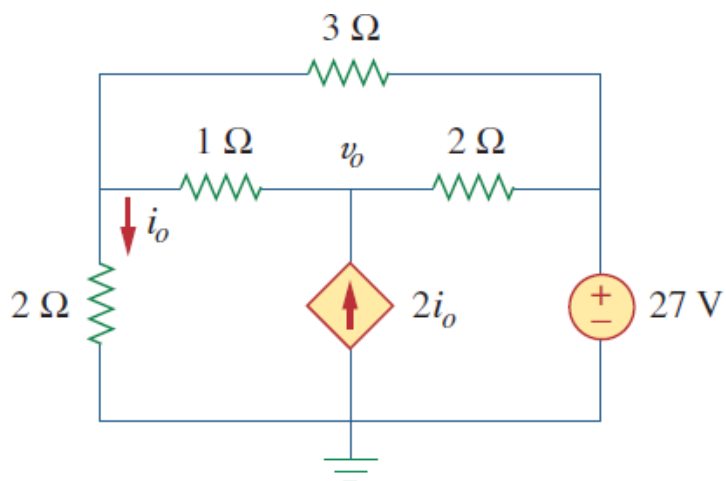
2. Find  $v_o$  and  $i_o$  in the circuit shown below:



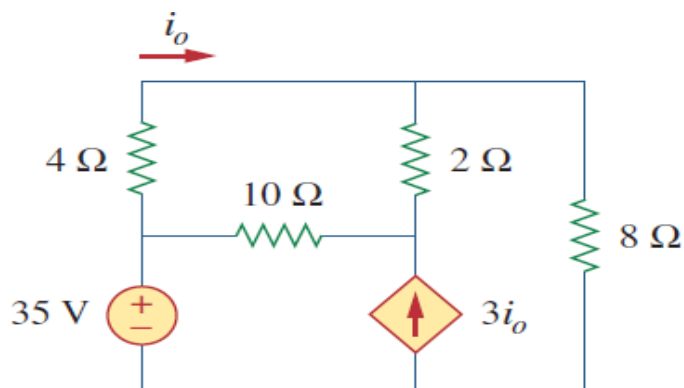
3. Use mesh analysis to find the current  $i_o$  in the circuit given below:



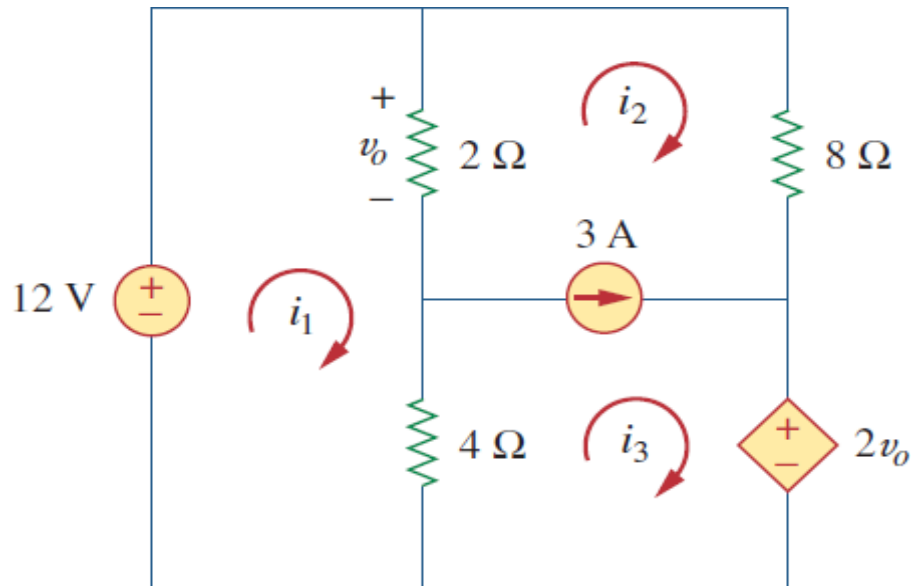4. Use mesh analysis to find  $i_1$ ,  $i_2$ , and  $i_3$  in the circuit shown below:




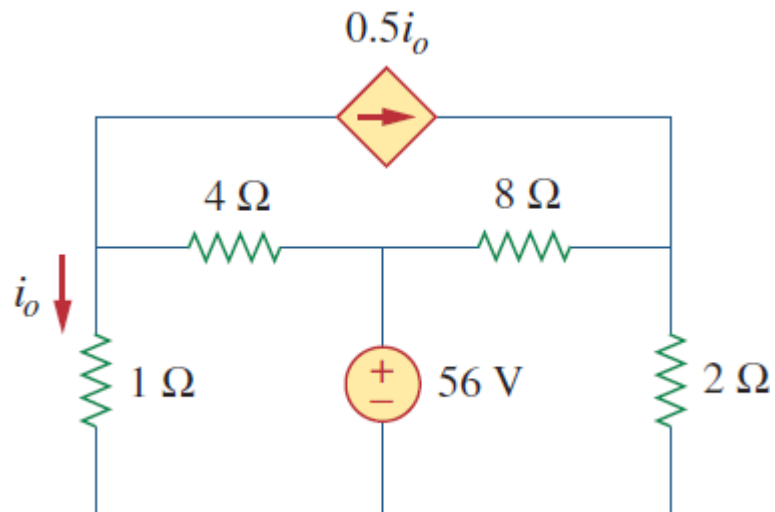5. Calculate the **power dissipated** in **each resistor** in the circuit given below. Use Mesh Analysis.




## Source Transformation

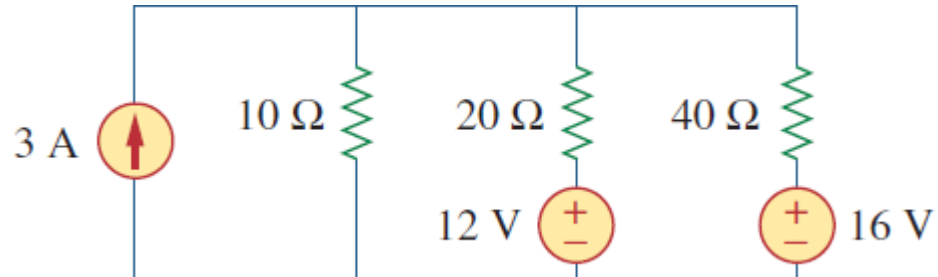
6. Use source transformation to reduce the circuit in the figure below to a single voltage source in series with a single resistor.



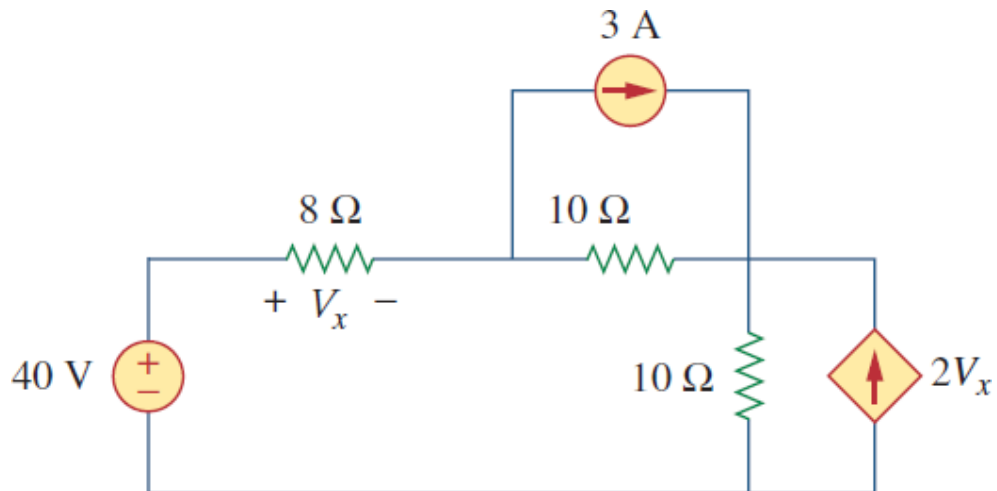
7. Use source transformation to find the voltage  $V_x$  in the circuit below.



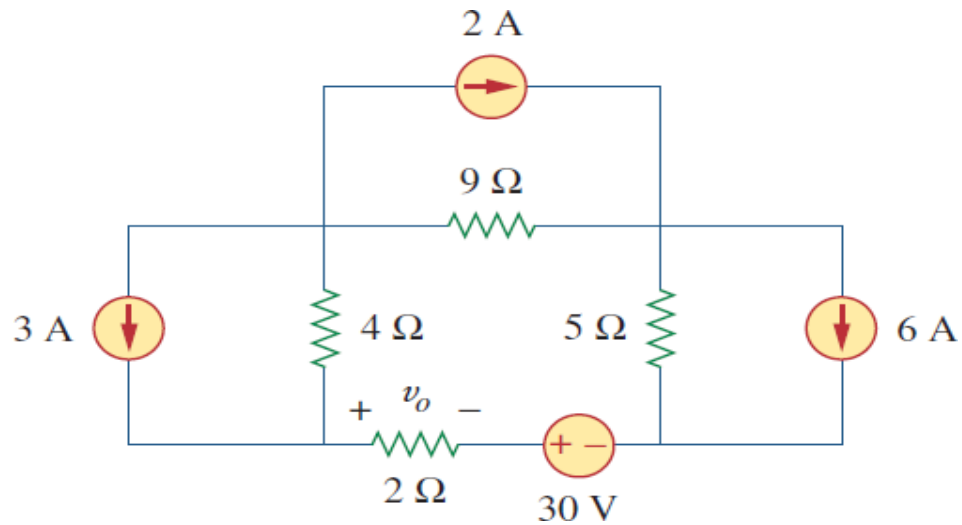8. Obtain  $v_o$  in the circuit shown below using source transformation.



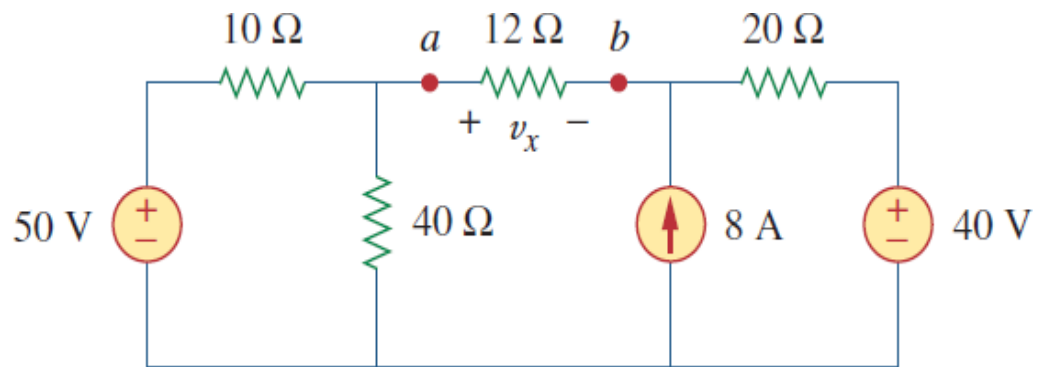9. Apply source transformation to find  $v_x$  in the circuit below.



10. Use source transformation to find  $v_o$  in the circuit given below.

