
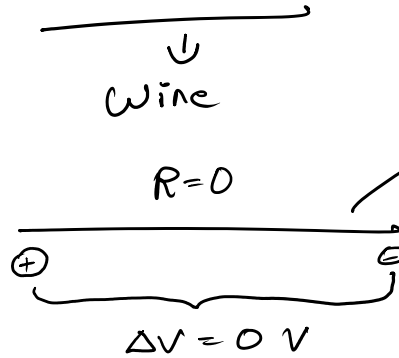


Lecture 4


Monday, February 14, 2022 9:40 AM

Circuit Symbols

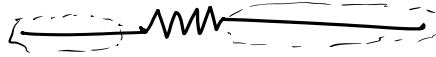


$$G = \frac{1}{R} = \frac{1}{0} = \infty$$

Continuous Piece of Wire → Node

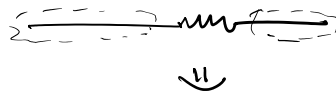

Discontinuous

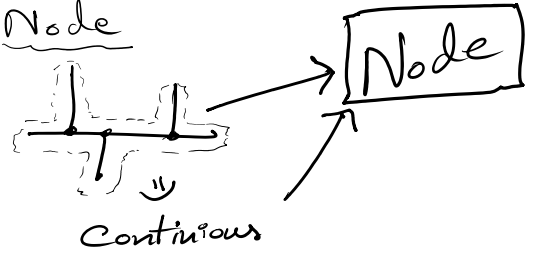


Rules


1. 1 Node \longrightarrow 1 voltage

2. 1 circuit component \longrightarrow 1 current flow.


Circuit component

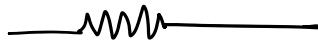


2 terminal

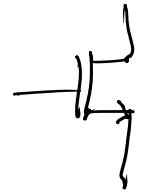


3 terminal

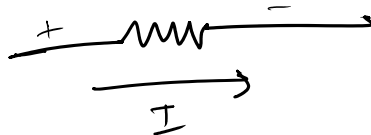

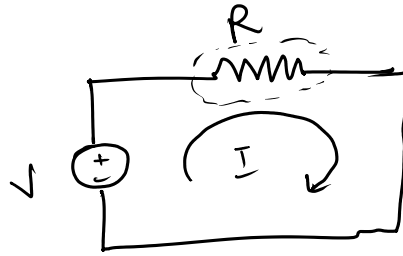
I-V Characteristics → Important Property of Circuit elements


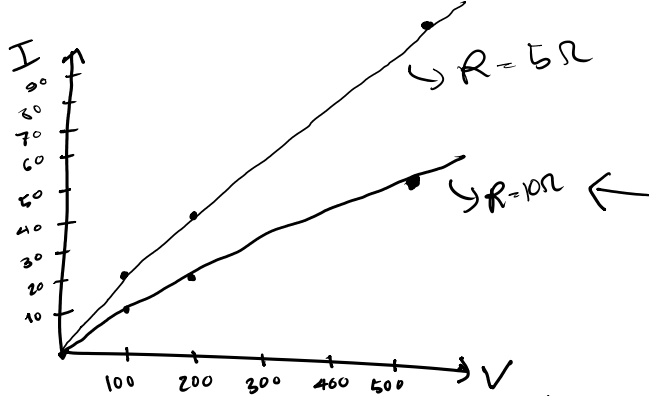
$$\left. \begin{aligned} V &= IR \\ \Rightarrow I &= \frac{V}{R} \end{aligned} \right\} \begin{aligned} V &= 0 \text{ V} \\ I &= 0 \text{ A} \end{aligned}$$



R	V	I
10Ω	100 V	10 A
10Ω	200 V	20 A
10Ω	500 V	50 A
5Ω	100 V	20 A
5Ω	200 V	40 A
5Ω	500 V	100 A


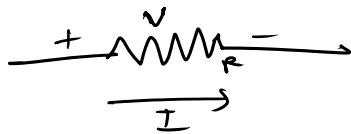


I-V Characteristics of Resistance
↓


Bottom line

- I changes proportionately with V
- Slope increases with decreasing R

Passive Sign Convention

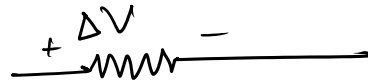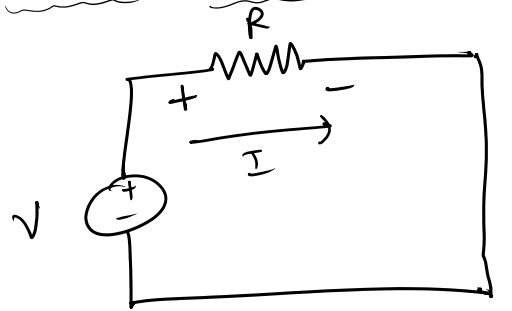

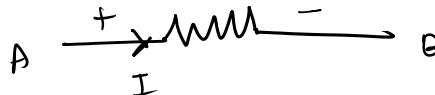
$$\Rightarrow \Delta V = V_+ - V_- \rightarrow \text{Always Voltage (positive terminal)} \\ - \text{Voltage (negative terminal)}$$




$$I_{(+ \rightarrow -)}$$

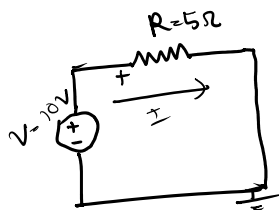H.W \rightarrow Passive sign convention in Power






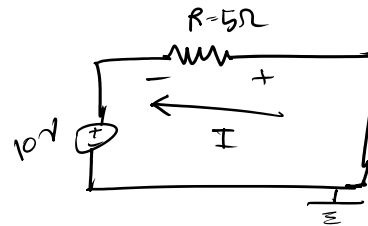
$$\begin{aligned} \Delta V &= V_+ - V_- \\ &= 10 - 0 \\ &= 10 \text{ V} \\ I &= \frac{\Delta V}{R} = \frac{10}{5} \\ &= 2 \text{ A} \end{aligned}$$



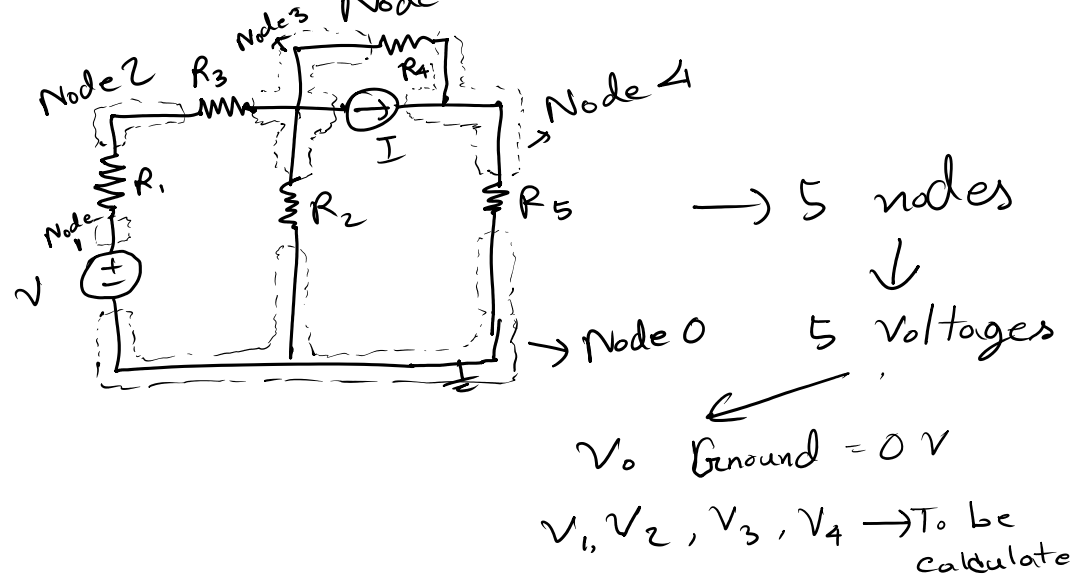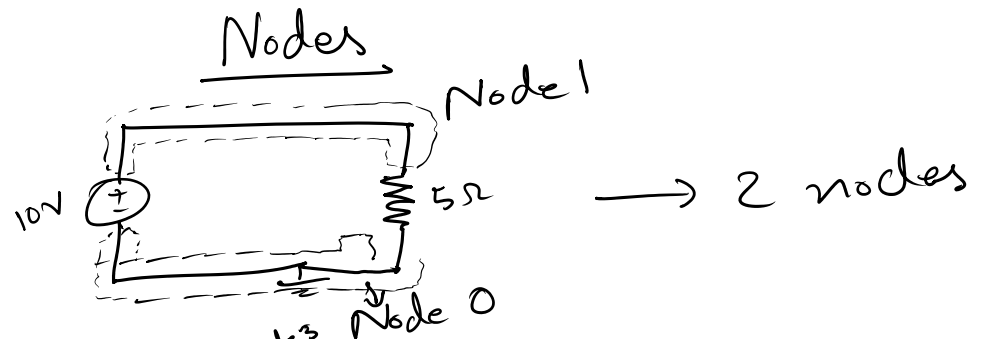
$$\begin{aligned} \Delta V &= V_+ - V_- \\ &= 0 - 10 \\ &= -10 \text{ V} \\ I &= \frac{\Delta V}{R} = \frac{-10}{5} \\ &= -2 \text{ A} \end{aligned}$$





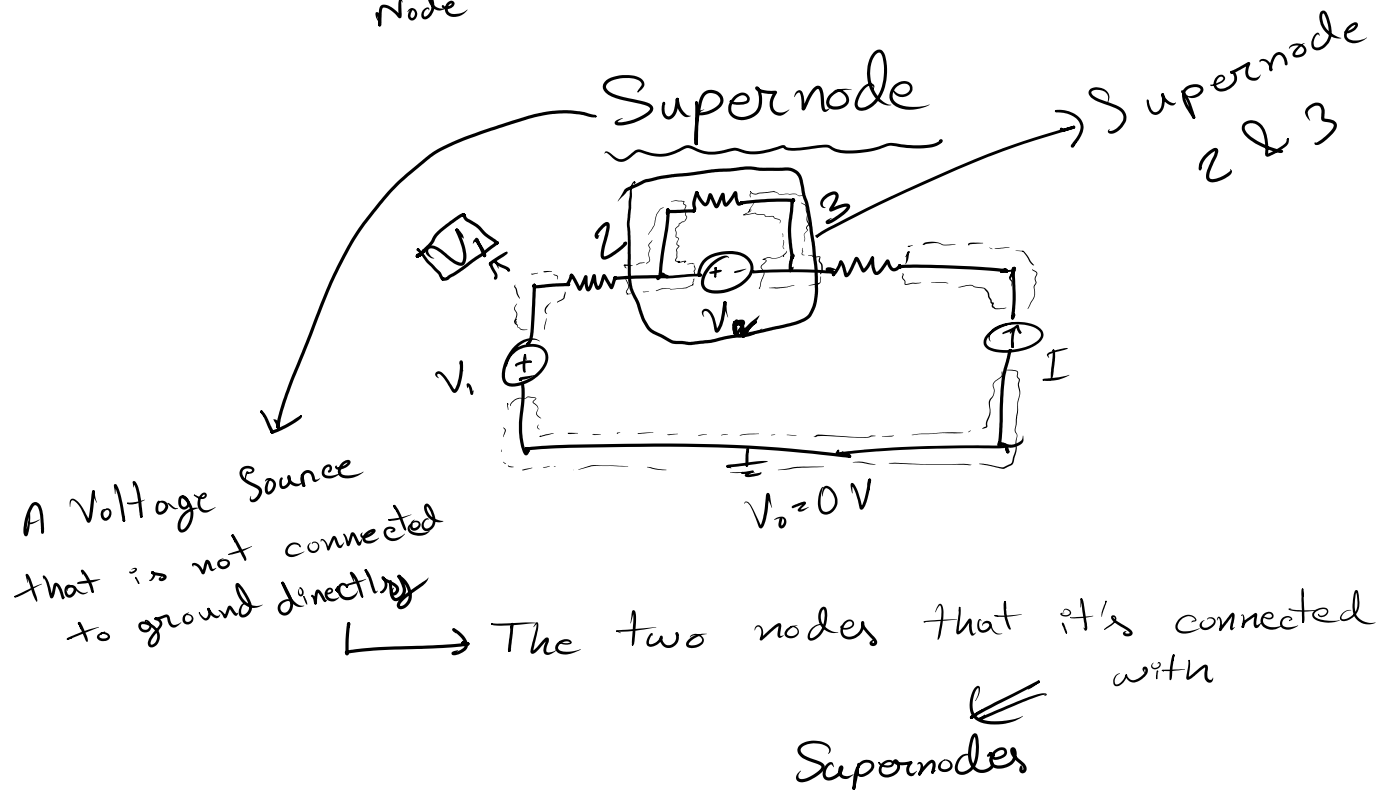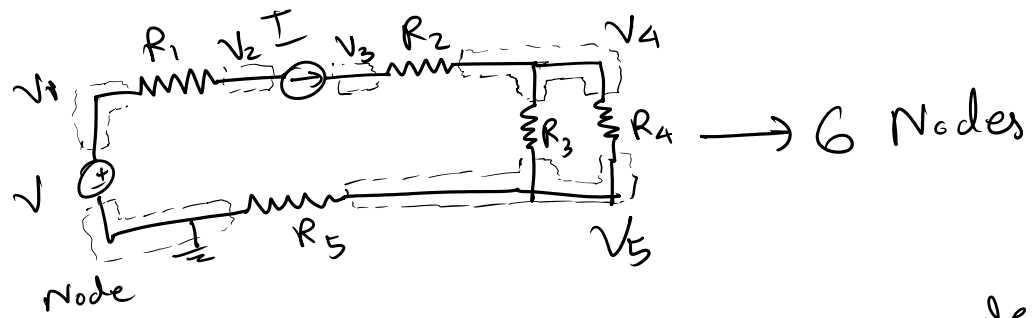

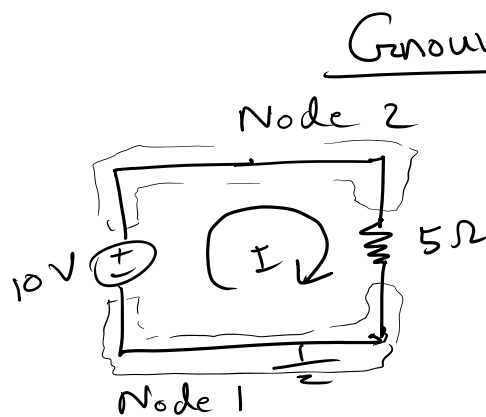

$$V_1, V_2$$

$$\downarrow \quad \downarrow$$

$$N_1 \quad N_2$$

$$V_2 - V_1 = 10 \text{ V} \quad \text{--- (i)}$$


$$V_1 = 0 \text{ V}$$

$$V_2 = 10 \text{ V}$$

$$I = \frac{V_2 - V_1}{R}$$

$$= \frac{10 \text{ V}}{5 \Omega}$$

$$= 2 \text{ A}$$

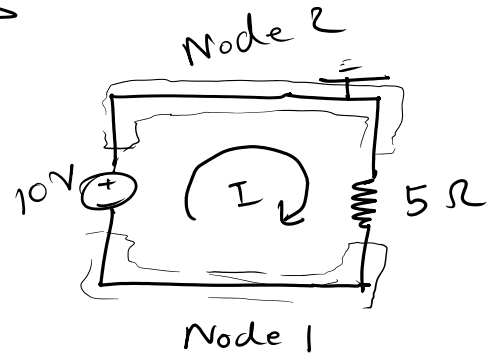

$$V_2 - V_1 = 10 \text{ V} \quad \text{--- (i)}$$

$$V_2 = 0 \text{ V}$$

$$-V_1 = 10 \text{ V}$$

$$\Rightarrow V_1 = -10 \text{ V}$$

$$I = \frac{V_2 - V_1}{R}$$

$$= \frac{10 \text{ V}}{5 \Omega}$$

$$= 2 \text{ A}$$

\therefore We work with differences of voltages, not absolute values.

So, we need a reference

Ground